



CSE112

**COMPUTER ORGANIZATION AND
ARCHITECTURE**

SOPHOMORE CESS

SPRING 2023

MAJOR TASK

Team members	ID
Mohamed Salah Fathy	21P0117
Seif Yasser Ahmed	21P0102
Youssef Tamer Hossam	21P0138
Gaser Zaghlol Hassan	21P0052
Ali Tarek Abdelmonim	21P0123

Table of Contents

Phase 1	3
Introduction:	5
Phase 1 requirements:	5
Modules' Codes:	6
ALU module:.....	6
Multiplexer (MUX) module:	7
Decoder module:	8
Flop Register module:	9
Register File module:.....	10
<i>Register file RTL schematic:</i>	10
R Format Module:	11
Code Description:.....	12
PHASE 2	16
Phase 2 Requirements:	16
Steps:.....	16
Modules' Codes:	18
Data path:.....	18
ALU decoder:.....	19
Main decoder:.....	21
Controller unit:.....	22
MIPS:	23
Main module:.....	24
Main module_tb(test bench):	25
Main module test bench results:	26
Adder:.....	28
Shifter:.....	29
Sign extend:.....	30
MUX 5 bits:.....	31
Instruction memory:	32
Data memory:	33
Code description:	34
Acknowledgement	35

List of Figures:

Figure 1: ALU VHDL code.....	6
Figure 2: ALU RTL	6
Figure 3: ALU RTL	6
Figure 4: MUX VHDL code	7
Figure 5 : MUX VHDL code	7
Figure 6 : MUX RTL.....	7
Figure 7 : Decoder VHDL Code	8
Figure 8 : Decoder VHDL Code	8
Figure 9 : Decoder RTL	8
Figure 10 : Decoder RTL	8
Figure 11 : Flop Register VHDL Code.....	9
Figure 12 : Flop Register RTL	9
Figure 13:reg file code2.....	10
Figure 14:reg file code1.....	10
Figure 15: Register File RTL	10
Figure 16 : Register File RTL	10
Figure 17 : R-Format VHDL Code.....	11
Figure 18 : R-Format RTL.....	11
Figure 19 : R-Format RTL.....	11
Figure 20: Main Module Pack (mainmodulepack)	12
Figure 21	13
Figure 22	13
Figure 23	14
Figure 24	14
Figure 25	15
Figure 26:cpu design	16
Figure 27:test case	17
Figure 28:data path code1	18
Figure 29:data path code2	18
Figure 30:data path RTL schematic	19
Figure 31:ALU decoder code	19
Figure 32:ALU decoder RTL schematic	20
Figure 33:main decoder code	21
Figure 34:main decoder RTL schematic	21
Figure 35:controller unit code.....	22
Figure 36:controller unit RTL schematic	22
Figure 37:mips code	23
Figure 38:mips RTL schematic.....	23
Figure 39:main module code	24
Figure 40:main module RTL schematic	24
Figure 41:main module test bench code1	25
Figure 42:main module test bench code2	25

Figure 43:main module test bench simulation	26
Figure 44: INSTRUCTIONS 6-10: 2 ND 5 CYCLES.....	26
Figure 45: INSTRUCTIONS 1-5: 1ST 5 CYCLES	26
Figure 46: INSTRUCTIONS 11-15: 3 RD 5 CYCLES.....	27
Figure 47: LAST INSTRUCTION: CYCLE # 16	27
Figure 48:adder code	28
Figure 49:adder RTL schematic	28
Figure 50:shifter code	29
Figure 51:shifter RTL schematic	29
Figure 52:sign extend code	30
Figure 53:sign extend RTL schematic	30
Figure 54:MUX code.....	31
Figure 55:MUX RTL schematic.....	31
Figure 56:Imem code	32
Figure 57:Imem RTL schematic	32
Figure 58:dmem code	33
Figure 59:dmem RTL schematic	33
Figure 60:ALU decoder table.....	34
Figure 61:Main decoder table.....	34

PHASE 1

Introduction:

This project's requirement is to design a MIPS processor using VHDL that illustrates a basic computer system by simulating the data and control paths, it's done in two phases.

Phase 1 requirements:

1- Implement the MIPS register file that reads simultaneously from two registers and write into another. The implementation should follow the internal logic design of the register file:

- The amin module should be called "RegisterFile".
- The entity should contain the following:
 - **read_sel1** : in std_logic_vector(4 downto 0)
 - **read_sel2** : in std_logic_vector(4 downto 0)
 - **write_sel** : in std_logic_vector(4 downto 0)
 - **write_ena** : in std_logic
 - **clk**: in std_logic
 - **write_data**: in std_logic_vector(31 downto 0)
 - **data1**: out std_logic_vector(31 downto 0)
 - **data2**: out std_logic_vector(31 downto 0)

2- Modify the 32-bit full ALU:

- ALU functional specifications:

ALU Op	Function
0000	AND
0001	OR
0010	ADD
0110	SUB
1100	NOR

- The entity should contain the following:
 - data1: in std_logic_vector (31 downto 0)
 - data2: in std_logic_vector (31 downto 0)
 - aluop: in std_logic_vector (3 downto 0)
 - dataout: out std_logic_vector (31 downto 0)
 - zflag: out std_logic

3- Connect the already-built modules including register file, ALU, to design a simple MIPS CPU Using VHDL. The proposed CPU should be able to perform certain instructions: R-type (AND, OR, ADD, SUB, SLT and NOR).

- The datapath entity should contain the following:
 - Clk, reset : in STD_LOGIC
 - Instr: in STD_LOGIC_VECTOR (31 downto 0)
 - Aluoperation: in STD_LOGIC_VECTOR (3 downto 0)

- Zero: out STD_LOGIC
- Regwrite: in STD_LOGIC
- Aluout: buffer STD_LOGIC_VECTOR (31 downto 0)

Modules' Codes:

ALU module:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4  use IEEE.NUMERIC_STD.ALL;
5  entity ALU is
6      Port ( data1 : in std_logic_vector(31 downto 0);
7            data2 : in std_logic_vector(31 downto 0);
8            aluop : in std_logic_vector(3 downto 0);
9            dataout: out std_logic_vector(31 downto 0);
10           zflag: out std_logic);
11 end ALU;
12 architecture Behavioral of ALU is
13
14     Signal result : std_logic_vector(31 downto 0);
15 begin
16
17     process(data1 , data2,aluop)
18     begin
19         case aluop is
20             when "0000" => --AND
21                 result <= data1 and data2;
22             when "0001" => --OR
23                 result <= data1 or data2;
24             when "0010" => --ADD
25                 result <= std_logic_vector(unsigned(data1) + unsigned(data2));
26             when "0110" => --SUB
27                 result <= std_logic_vector(unsigned(data1) - unsigned(data2));
28             when "1100" => --NOR
29                 result <= data1 nor data2;
30             when others => null;
31         end case;
32     end process;
33     dataout<=result;
34     zflag <='1' when result =x"00000000" else
35         '0';
36 end Behavioral;

```

Figure 1: ALU VHDL code

ALU RTL schematic:

 


Figure 3: ALU RTL

 


Figure 2: ALU RTL

Multiplexer (MUX) module:

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity MUX is
5     Port ( A0,A1,A2,A3,A4,A5,A6,A7,A8,A9,A10,A11,A12,A13,A14,A15,A16,A17,A18,A19,A20,A21,A22,A23,A24,A25,A26,A27,A28,A29,A30,A31 : in STD_LOGIC_VECTOR (31 downto 0);
6           S : in STD_LOGIC_VECTOR (4 downto 0));
7 end MUX;
8
9 architecture Behavioral of MUX is
10
11
12 begin
13     Z1 <=
14     A0 when S="00000" else
15     A1 when S="00001" else
16     A2 when S="00010" else
17     A3 when S="00011" else
18     A4 when S="00100" else
19     A5 when S="00101" else
20     A6 when S="00110" else
21     A7 when S="00111" else
22     A8 when S="01000" else
23     A9 when S="01001" else
24     A10 when S="01010" else
25     A11 when S="01011" else
26     A12 when S="01100" else
27     A13 when S="01101" else
28     A14 when S="01110" else
29     A15 when S="01111" else
30     A16 when S="10000" else
31     A17 when S="10001" else
32     A18 when S="10010" else
33     A19 when S="10011" else
34     A20 when S="10100" else
35     A21 when S="10101" else
36     A22 when S="10110" else
37     A23 when S="10111" else
```

Figure 4: MUX VHDL code

```
29     A15 when S="01111" else
30     A16 when S="10000" else
31     A17 when S="10001" else
32     A18 when S="10010" else
33     A19 when S="10011" else
34     A20 when S="10100" else
35     A21 when S="10101" else
36     A22 when S="10110" else
37     A23 when S="10111" else
38     A24 when S="11000" else
39     A25 when S="11001" else
40     A26 when S="11010" else
41     A27 when S="11011" else
42     A28 when S="11100" else
43     A29 when S="11101" else
44     A30 when S="11110" else
45     A31 when S="11111" ;
46
47 end Behavioral;
48
```

MUX RTL schematic:

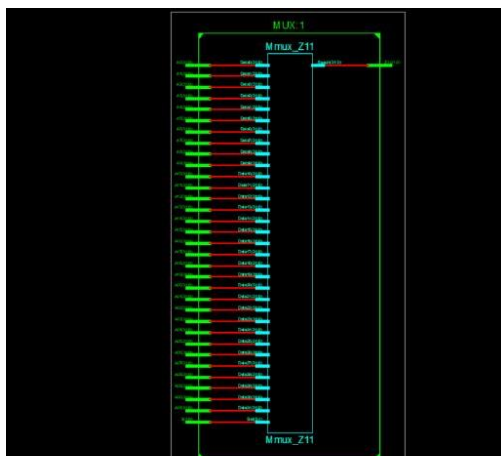


Figure 6 : MUX RTL

Decoder module:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  entity Decodermodule is
4      Port ( a : in  STD_LOGIC_VECTOR (4 downto 0);
5            y : out STD_LOGIC_VECTOR (31 downto 0));
6  end Decodermodule;
7
8  architecture Behavioral of Decodermodule is
9
10 begin
11     process(a)
12     begin
13         if (a="00000") then
14             y <= x"000000001";
15         elsif (a="00001") then
16             y <= x"000000002";
17         elsif (a="00010") then
18             y <= x"000000004";
19         elsif (a="00011") then
20             y <= x"000000008";
21         elsif (a="00100") then
22             y <= x"000000010";
23         elsif (a="00101") then
24             y <= x"000000020";
25         elsif (a="00110") then
26             y <= x"000000040";
27         elsif (a="00111") then
28             y <= x"000000080";
29         elsif (a="01000") then
30             y <= x"000000100";
31         elsif (a="01001") then
32             y <= x"000000200";
33         elsif (a="01010") then
34             y <= x"000000400";
35         elsif (a="01011") then
36             y <= x"000000800";

```

Figure 7 : Decoder VHDL Code

```

36         y <= x"000000800";
37     elsif (a="01100") then
38         y <= x"000001000";
39     elsif (a="01101") then
40         y <= x"000002000";
41     elsif (a="01110") then
42         y <= x"000004000";
43     elsif (a="01111") then
44         y <= x"000008000";
45     elsif (a="10000") then
46         y <= x"000010000";
47     elsif (a="10001") then
48         y <= x"000020000";
49     elsif (a="10010") then
50         y <= x"000040000";
51     elsif (a="10011") then
52         y <= x"000080000";
53     elsif (a="10100") then
54         y <= x"000100000";
55     elsif (a="10101") then
56         y <= x"000200000";
57     elsif (a="10110") then
58         y <= x"000400000";
59     elsif (a="10111") then
60         y <= x"000800000";
61     elsif (a="11000") then
62         y <= x"001000000";
63     elsif (a="11001") then
64         y <= x"002000000";
65     elsif (a="11010") then
66         y <= x"004000000";
67     elsif (a="11011") then
68         y <= x"008000000";
69     elsif (a="11100") then
70         y <= x"001000000";
71     elsif (a="11101") then

```

Figure 8 : Decoder VHDL Code

Decoder RTL schematic:

 


Figure 9 : Decoder RTL

 


Figure 10 : Decoder RTL

Flop Register module:

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity FRegister is
5     Port ( d : in  STD_LOGIC_VECTOR (31 downto 0);
6           rst : in  STD_LOGIC;
7           clk : in  STD_LOGIC;
8           load : in  std_logic;
9           q : out  STD_LOGIC_VECTOR (31 downto 0));
10 end FRegister;
11
12 architecture Behavioral of FRegister is
13
14 begin
15     PROCESS(clk,rst,load,d)
16     begin
17         IF(rst='1')THEN
18             q<=(others=>'0');
19         ELSIF(clk'EVENT AND clk='1' and load='1')THEN
20             q<=d;
21         end if;
22     END PROCESS;
23
24 end Behavioral;
```

Figure 11 : Flop Register VHDL Code

Flop register RTL schematic:

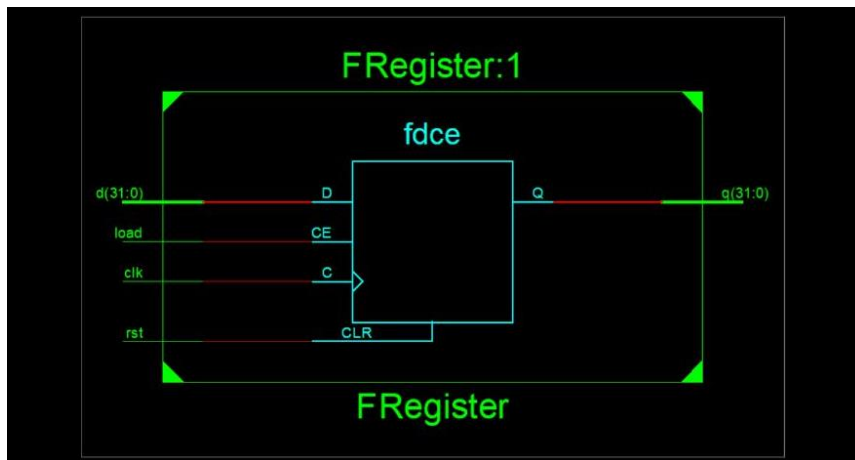


Figure 12 : Flop Register RTL

Register File module:

```

30 --library UNISIM;
31 --use UNISIM.VComponents.all;
32
33 entity RegisterFile is
34 port(
35   read_sel1 : in std_logic_vector(4 downto 0);
36   read_sel2 : in std_logic_vector(4 downto 0);
37   write_sel : in std_logic_vector(4 downto 0);
38   write_ena : in std_logic;
39   clk : in std_logic;
40   reset : in std_logic;
41   write_data : in std_logic_vector(31 downto 0);
42   data1 : out std_logic_vector(31 downto 0);
43   data2 : out std_logic_vector(31 downto 0);
44 );
45 end RegisterFile;
46
47 architecture Behavioral of RegisterFile is
48
49   signal out0 : std_logic_vector(31 downto 0);
50   signal out1 : std_logic_vector(31 downto 0);
51   signal out2 : std_logic_vector(31 downto 0);
52   signal out3 : std_logic_vector(31 downto 0);
53   signal out4 : std_logic_vector(31 downto 0);
54   signal out5 : std_logic_vector(31 downto 0);
55   signal out6 : std_logic_vector(31 downto 0);
56   signal out7 : std_logic_vector(31 downto 0);
57   signal out8 : std_logic_vector(31 downto 0);
58   signal out9 : std_logic_vector(31 downto 0);
59   signal out10 : std_logic_vector(31 downto 0);
60   signal out11 : std_logic_vector(31 downto 0);
61   signal out12 : std_logic_vector(31 downto 0);
62   signal out13 : std_logic_vector(31 downto 0);
63   signal out14 : std_logic_vector(31 downto 0);

```

Figure 14: reg file code1

```

108 signal load27 : std_logic;
109 signal load28 : std_logic;
110 signal load29 : std_logic;
111 signal load30 : std_logic;
112 signal load31 : std_logic;
113 signal dec_out : std_logic_vector(31 downto 0);
114
115
116 begin
117
118   load0 <= write_ena and dec_out(0);
119   load1 <= write_ena and dec_out(1);
120   load2 <= write_ena and dec_out(2);
121   load3 <= write_ena and dec_out(3);
122   load4 <= write_ena and dec_out(4);
123   load5 <= write_ena and dec_out(5);
124   load6 <= write_ena and dec_out(6);
125   load7 <= write_ena and dec_out(7);
126   load8 <= write_ena and dec_out(8);
127   load9 <= write_ena and dec_out(9);
128   load10 <= write_ena and dec_out(10);
129   load11 <= write_ena and dec_out(11);
130   load12 <= write_ena and dec_out(12);
131   load13 <= write_ena and dec_out(13);
132   load14 <= write_ena and dec_out(14);
133   load15 <= write_ena and dec_out(15);
134   load16 <= write_ena and dec_out(16);
135   load17 <= write_ena and dec_out(17);
136   load18 <= write_ena and dec_out(18);
137   load19 <= write_ena and dec_out(19);
138   load20 <= write_ena and dec_out(20);
139   load21 <= write_ena and dec_out(21);
140   load22 <= write_ena and dec_out(22);
141   load23 <= write_ena and dec_out(23);
142   load24 <= write_ena and dec_out(24);

```

Figure 13: reg file code2

Register file RTL schematic:



Figure 16 : Register File RTL

 


Figure 15: Register File RTL

R Format Module:

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use work.mainmodulepack.all;
5
6 entity Phase1module is
7 port(
8   clk, reset: in STD_LOGIC;
9   instr: in STD_LOGIC_VECTOR(31 downto 0);
10  aluoperation: in STD_LOGIC_VECTOR(3 downto 0);
11  zero: out STD_LOGIC;
12  regwrite: in STD_LOGIC;
13  aluout : buffer STD_LOGIC_VECTOR(31 downto 0)
14 );
15 end Phase1module;
16
17 architecture Behavioral of Phase1module is
18
19   signal data1out : STD_LOGIC_VECTOR(31 downto 0);
20   signal data2out : STD_LOGIC_VECTOR(31 downto 0);
21
22 begin
23
24   RegFile : RegisterFile port map(instr(25 downto 21),instr(20 downto 16),instr(15 downto 11),regwrite,clk,aluout,data1out,data2out);
25   ALU1 : ALU port map(data1out,data2out,aluoperation,aluout,zero);
26 end Behavioral;
27
28

```

Figure 17 : R-Format VHDL Code

R Format RTL Schematic:

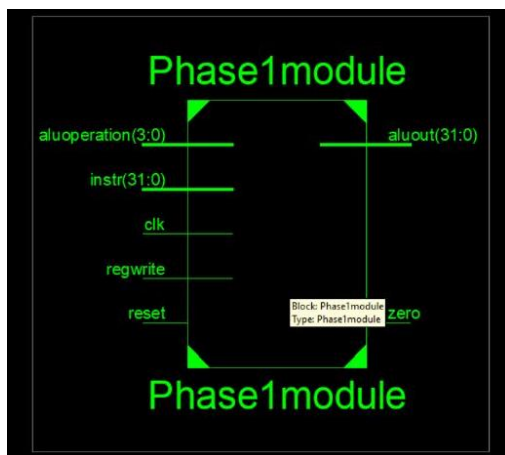


Figure 19 : R-Format RTL

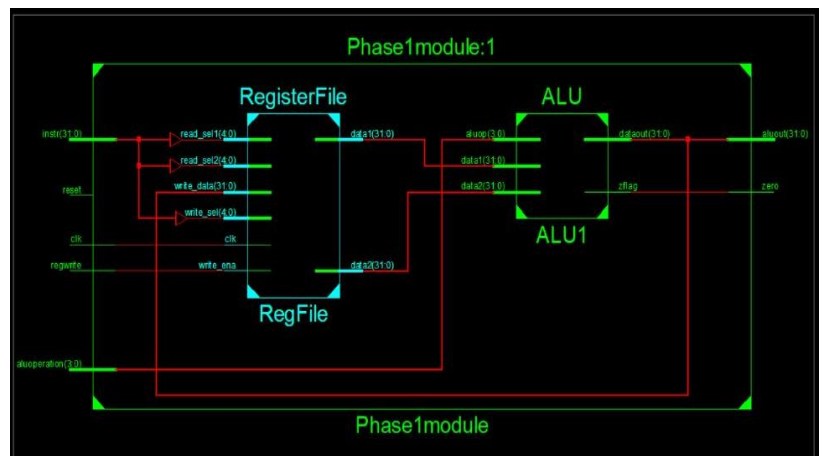


Figure 18 : R-Format RTL

Code Description:

- In Phase 1 of MIPS Processor Implementation using VHDL we implemented the R-Format Instructions only.
- We used Decoder, Multiplexers, and Flop Registers to implement the Register File
- We also implemented an ALU that has AND, OR ADD, SUB, and, NOR operations.
- The Register File has two modes which are read and write.
- In the write mode we used 32 Flop Register and a decoder.
- In the read mode we used 32 Flop Registers and 2 Multiplexers.
- We used all of these components by declaring them as a package named as mainmodulepack then, declaring them in other modules using use work.mainmodulepack.all
- The load function were implemented by implementing 32 Signals

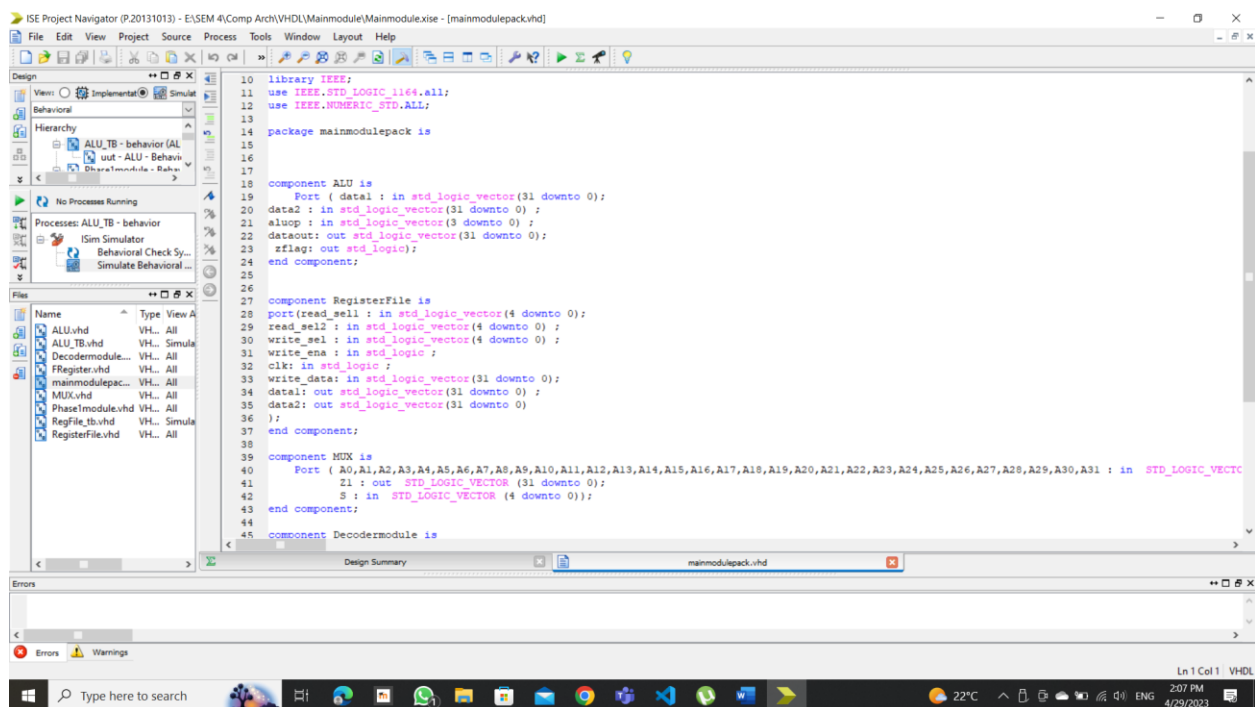


Figure 20: Main Module Pack (mainmodulepack)

Lab Goal! (Main Step)

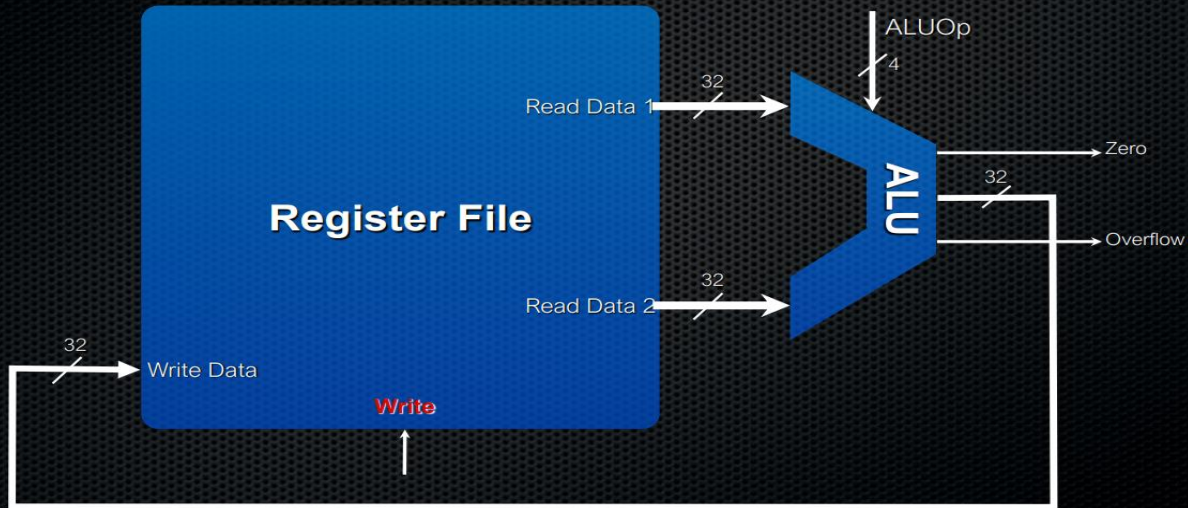


Figure 21

ALU Functional Specification

ALUOp	Function
0000	AND
0001	OR
0010	ADD
0110	SUB
1100	NOR

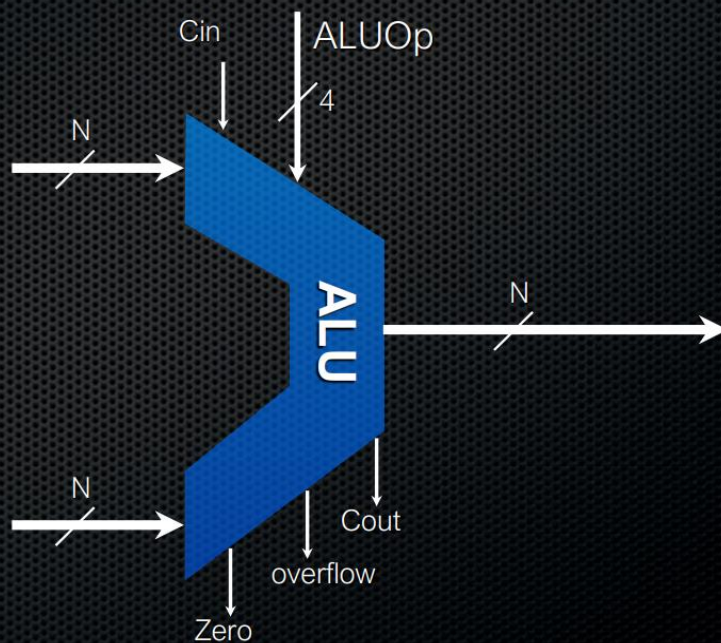


Figure 22

Register File - Reading

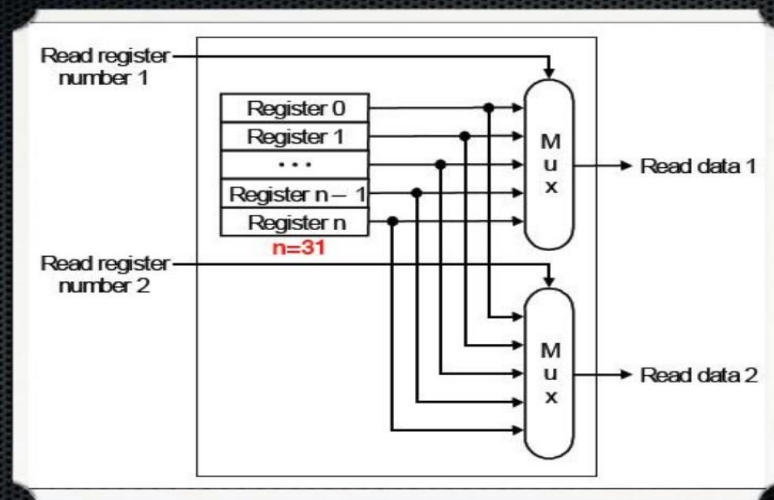


Figure 24

Register File - Writing

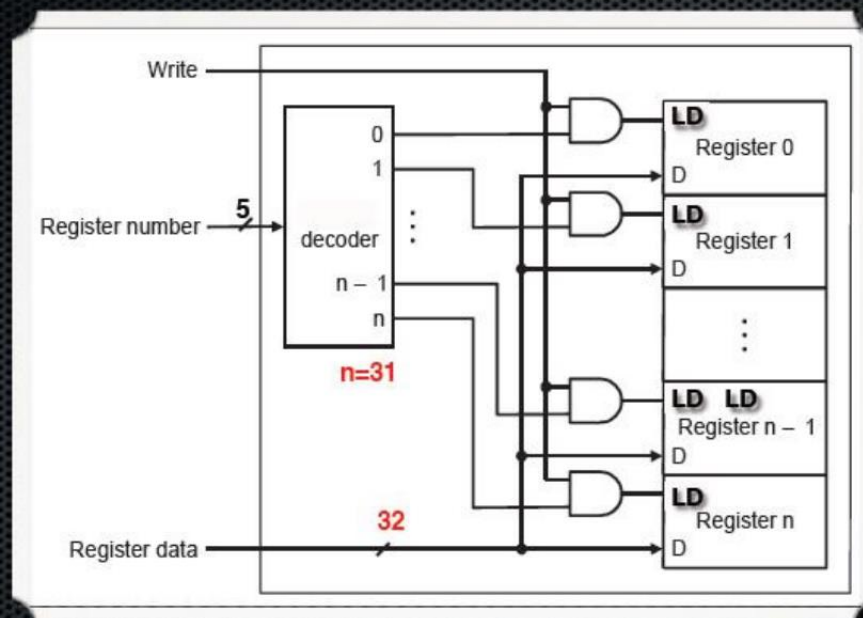


Figure 23

The MIPS Register File

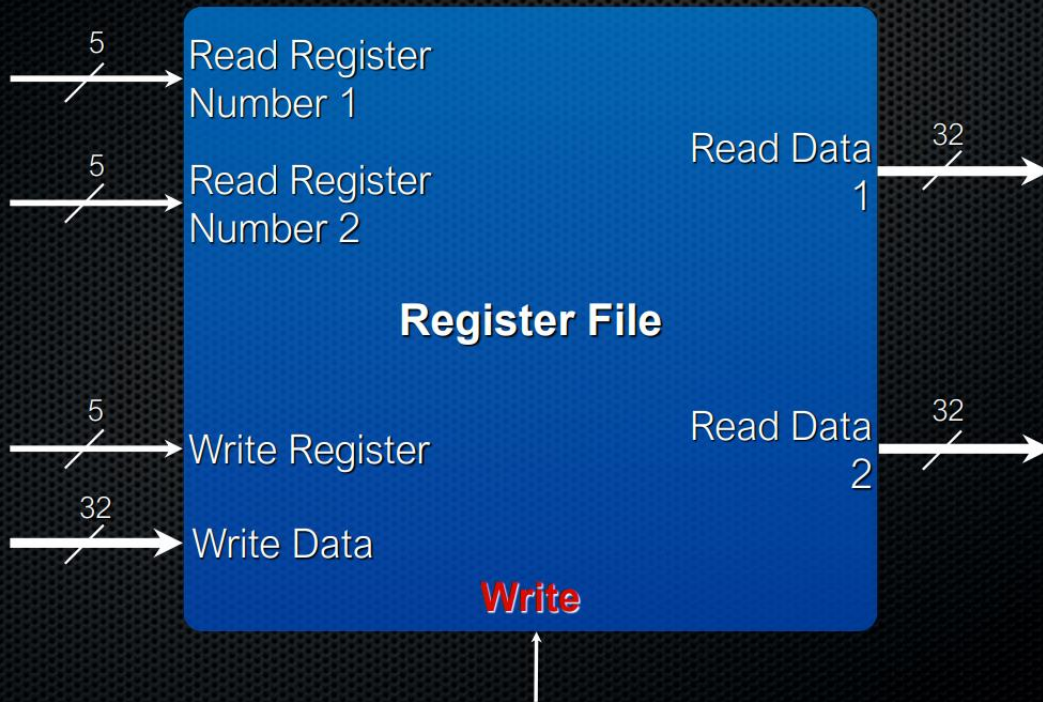


Figure 25

PHASE 2

Phase 2 Requirements:

To Modify the MIPS CPU as to be able to perform not only R instructions, but also I-type (lw, sw, beq) and J instruction.

Steps:

1. Implement the control module, which is responsible for all the control signals.
2. Implement the Mips module by connecting the datapath with the control module.
3. Connect the Mips module with instruction and data memory module together.
4. Then Fill the memory module by a simple program.
5. The CPU should be able to execute this program.
6. Simulate the results and check the final results.

This diagram shows the abstract CPU design.

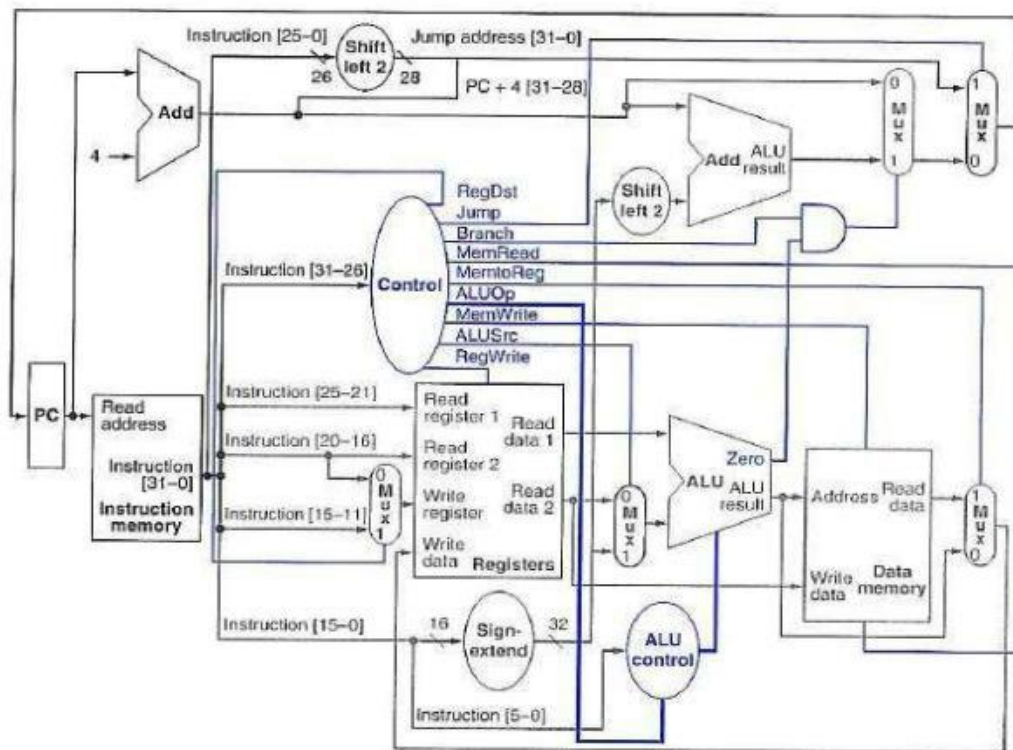


Figure 26:cpu design

7. The main module entity contains the following:

- CLK: IN STD_LOGIC;
- RST: IN STD_LOGIC;
- Writedata,dataadr: OUT STD_LOGIC_VECTOR(31 downto 0);
- memwrite: OUT STD_LOGIC;

8. Test Case:

```
main:    addi $2, $0, 5 # initialize $2 = 5 0 20020005
        addi $3, $0, 12 # initialize $3 = 12 4 2003000c
        addi $7, $3, -9 # initialize $7 = 3 8 2067fff7
        or $4, $7, $2 # $4 = (3 OR 5) = 7 c 00e22025
        and $5, $3, $4 # $5 = (12 AND 7) = 4 10 00642824
        add $5, $5, $4 # $5 = 4 + 7 = 11 14 00a42820
        beq $5, $7, end # shouldn't be taken 18 10a7000a
        slt $4, $3, $4 # $4 = 12 < 7 = 0 1c 0064202a
        beq $4, $0, around # should be taken 20 10800001
        addi $5, $0, 0 # shouldn't happen 24 20050000
around:  slt $4, $7, $2 # $4 = 3 < 5 = 1 28 00e2202a
        add $7, $4, $5 # $7 = 1 + 11 = 12 2c 00853820
        sub $7, $7, $2 # $7 = 12 - 5 = 7 30 00e23822
        sw $7, 68($3) # [80] = 7 34 ac670044
        lw $2, 80($0) # $2 = [80] = 7 38 8c020050
        j end # should be taken 3c 08000011
        addi $2, $0, 1 # shouldn't happen 40 20020001
end:     sw $2, 84($0) # write mem[84] = 7 44 ac020054
```

Test the MIPS processor.

add, sub, and, or, slt, addi, lw, sw, beq, j

If successful, it should write the value 7 to address 84

Figure 27:test case

Modules' Codes:

Data path:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use work.mainmodulepack.all;
4
5  entity DataPath is
6  port ( clk : in std_logic;
7        reset : in std_logic;
8        readdata : in std_logic_vector(31 downto 0);
9        instr : in std_logic_vector(31 downto 0);
10       memtoreg , pcsrc , alusrc , regwrite , regdst : in std_logic;
11       aluoperation : in std_logic_vector(3 downto 0);
12       zero : out std_logic;
13       pc : out std_logic_vector(31 downto 0);
14       jump : in std_logic;
15       aluout , writedata : out std_logic_vector(31 downto 0));
16 end DataPath;
17
18 architecture Behavioral of DataPath is
19
20   signal writereg : std_logic_vector(4 downto 0);
21   signal pcjump , pcnext , pcnextbr , pcplus4 , pcbranch : std_logic_vector(31 downto 0);
22   signal signimm , signimmsh : std_logic_vector(31 downto 0);
23   signal load : std_logic;
24   signal datalout : STD_LOGIC_VECTOR(31 downto 0);
25   signal data2out : STD_LOGIC_VECTOR(31 downto 0);
26   signal writedata1 : std_logic_vector(31 downto 0);
27   signal pcl : std_logic_vector(31 downto 0);
28   signal aluout1 : std_logic_vector(31 downto 0);
29   signal writedata2 : std_logic_vector(31 downto 0);
30 begin
31
32   load <= '1' ;
33
34   pc <= pcl ;
35
36   aluout <= aluout1 ;
37
38   writedata <= writedata2 ;
```

Figure 28:data path code1

```
36   aluout <= aluout1 ;
37   |
38   writedata <= writedata2 ;
39
40   pcjump <= pcplus4(31 downto 28) & instr(25 downto 0) & "00";
41
42   pcreg : FRegister port map( pcnext , reset , clk , load , pcl );
43
44   pcadd1: adder port map( pcl , X"00000004" , pcplus4);
45
46   immsh : Shifter port map( signimm , signimmsh);
47
48   pcadd2 : adder port map( pcplus4 , signimmsh , pcbranch );
49
50   pcbrmux : MUX2x1 port map(pcplus4 , pcbranch , pcnextbr , pcsrc );
51
52   pcmux : MUX2x1 port map(pcnextbr , pcjump , pcnext , jump );
53
54   signext : SignedBits port map(instr(15 downto 0) , signimm );
55
56   regfilemux : MUX2x15bits port map(instr(20 downto 16) , instr(15 downto 11) , writereg , regdst);
57   RegFile : RegisterFile port map(instr(25 downto 21),instr(20 downto 16),writereg,regwrite,clk,writedata1,datalout, writedata2 );
58
59   alumux : MUX2x1 port map( writedata2 , signimm , data2out , alusrc );
60   ALU1 : ALU port map(datalout , data2out , aluoperation , aluout1 ,zero);
61
62   memregmux : MUX2x1 port map(aluout1 , readdata , writedata1 , memtoreg);
63
64
65
66 end Behavioral;
67
```

Figure 29:data path code2

Data path RTL schematic:

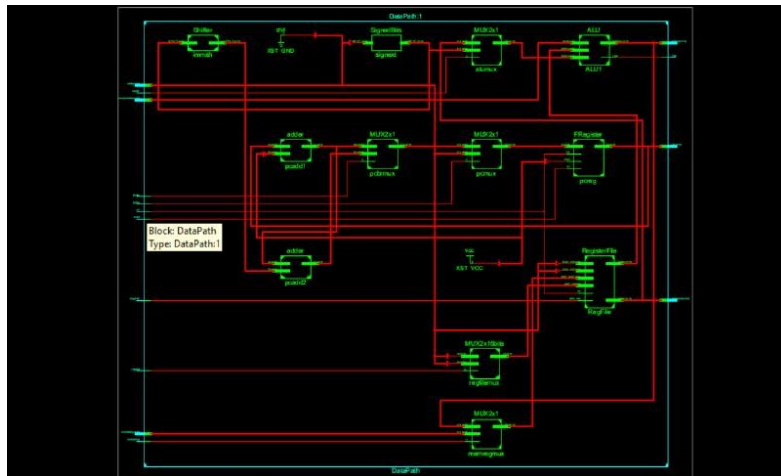


Figure 30: data path RTL schematic

ALU decoder:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity AluDecoder is
5  port(funcnt : in std_logic_vector(5 downto 0);
6        aluop : in std_logic_vector(1 downto 0);
7        alucontrol : out std_logic_vector(3 downto 0));
8  end AluDecoder;
9
10 architecture Behavioral of AluDecoder is
11
12 begin
13 process(aluop , funcnt)
14 begin
15 case aluop is
16   when "00" => alucontrol <="0010";
17   when "01" => alucontrol <="0110";
18   when others =>
19     case funcnt is
20       when "100000" => alucontrol <= "0010" ;
21       when "100010" => alucontrol <= "0110" ;
22       when "100100" => alucontrol <= "0000" ;
23       when "100101" => alucontrol <= "0001" ;
24       when "101010" => alucontrol <= "0111" ;
25       when others => alucontrol <= "----";
26     end case ;
27   end case ;
28 end process;
29
30 end Behavioral;
31
32

```

Figure 31:ALU decoder code

ALU decoder RTL schematic:

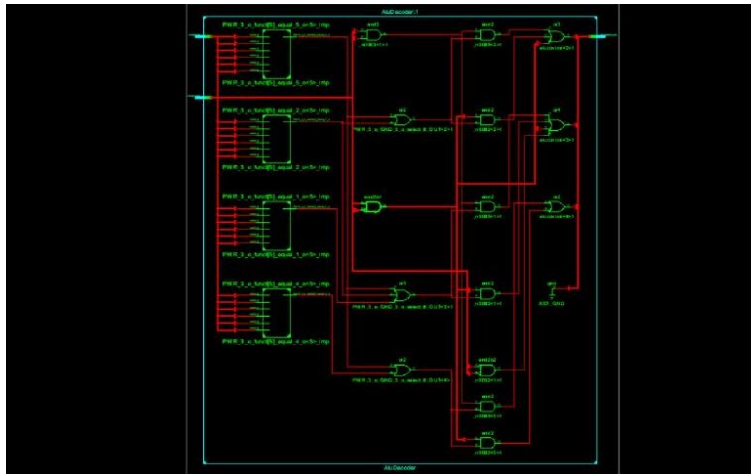


Figure 32:ALU decoder RTL schematic

Main decoder:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity MainDecoder is
5  port ( op : in std_logic_vector(5 downto 0);
6        memtoreg , memwrite , branch , alusrc , regdst , regwrite , jump : out std_logic ;
7        aluop : out std_logic_vector(1 downto 0));
8  end MainDecoder;
9
10 architecture Behavioral of MainDecoder is
11 signal controls : std_logic_vector(8 downto 0);
12 begin
13
14 process(op)
15 begin
16 case op is
17   when "000000" => controls <= "1100000010" ;
18   when "100011" => controls <= "1010010000" ;
19   when "101011" => controls <= "0010100000" ;
20   when "000100" => controls <= "0001000001" ;
21   when "001000" => controls <= "1010000000" ;
22   when "000010" => controls <= "0000001000" ;
23   when others => controls <= "-----";
24 end case ;
25 end process;
26 (regwrite , regdst , alusrc , branch , memwrite , memtoreg , jump , aluop(1),aluop(0))<= controls;
27 end Behavioral;
28
29
```

Figure 33:main decoder code

Main decoder RTL schematic:

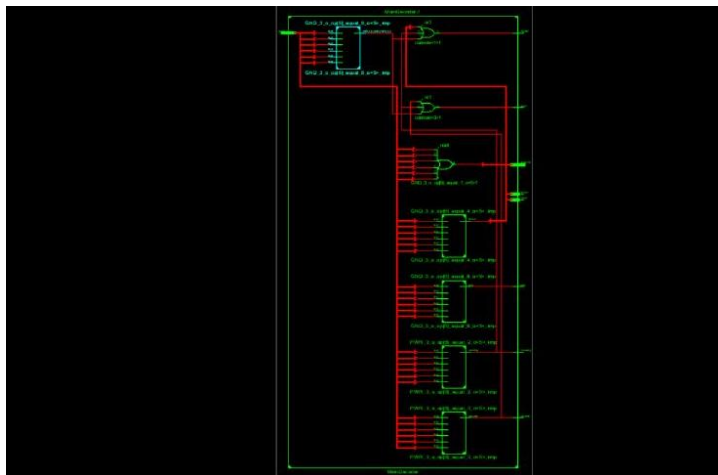


Figure 34:main decoder RTL schematic

Controller unit:

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use work.ControllerPackage.all;
5
6 entity ControllerUnit is
7 port( op , funct : in std_logic_vector(5 downto 0);
8       zero : in std_logic ;
9       memtoreg , memwrite , pcsrc , alusrc , regdst , regwrite , jump : out std_logic;
10      alucontrol : out std_logic_vector(3 downto 0));
11 end ControllerUnit;
12
13 architecture Behavioral of ControllerUnit is
14 signal aluop : std_logic_vector(1 downto 0);
15 signal branch : std_logic ;
16 begin
17
18 maindec1 : MainDecoder port map(op , memtoreg , memwrite , branch , alusrc , regdst , regwrite , jump , aluop);
19 Aludec1 : AluDecoder port map(funct , aluop , alucontrol);
20 pcsrc <= branch and zero ;
21
22 end Behavioral;
23
24

```

Figure 35:controller unit code

Controller unit RTL schematic:

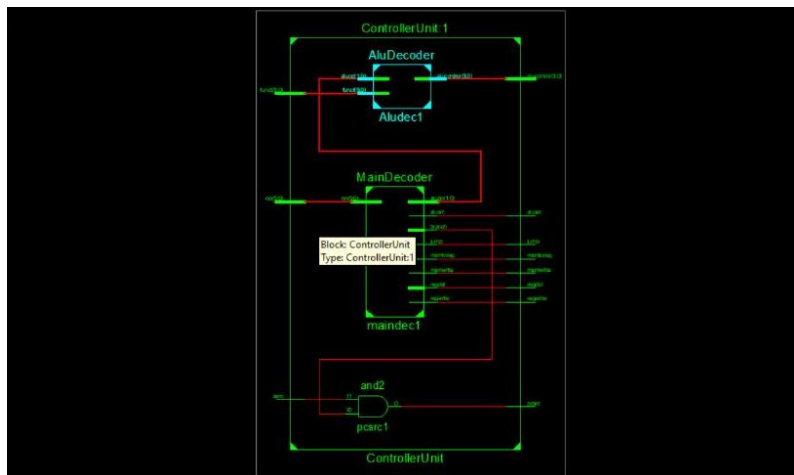


Figure 36:controller unit RTL schematic

MIPS:

```

4
5
6 library IEEE;
7 use IEEE.STD_LOGIC_1164.ALL;
8 use work.mainmodulepack.all;
9
10 entity MIPS is
11 port( clk , reset : in std_logic;
12       pc : out std_logic_vector(31 downto 0);
13       instr : in std_logic_vector(31 downto 0);
14       memwrite : out std_logic;
15       aluout , writedata : out std_logic_vector(31 downto 0);
16       readdata : in std_logic_vector(31 downto 0));
17 end MIPS;
18
19 architecture Behavioral of MIPS is
20
21 signal memtoreg , alusrc , regdst , regwrite , jump , pcsrc: std_logic;
22 signal zero : std_logic;
23 signal alucontrol : std_logic_vector(3 downto 0);
24
25 begin
26
27 Controller : ControllerUnit port map(instr(31 downto 26) , instr(5 downto 0) , zero , memtoreg , memwrite , pcsrc , alusrc , regdst , regwrite , jump , alucontrol);
28
29 datapath1 : DataPath port map ( clk , reset , readdata , instr , memtoreg , pcsrc , alusrc , regwrite , regdst , alucontrol , zero , pc , jump , aluout , writedata );
30
31 end Behavioral;
32
33

```

Figure 37:mips code

MIPS RTL schematic:

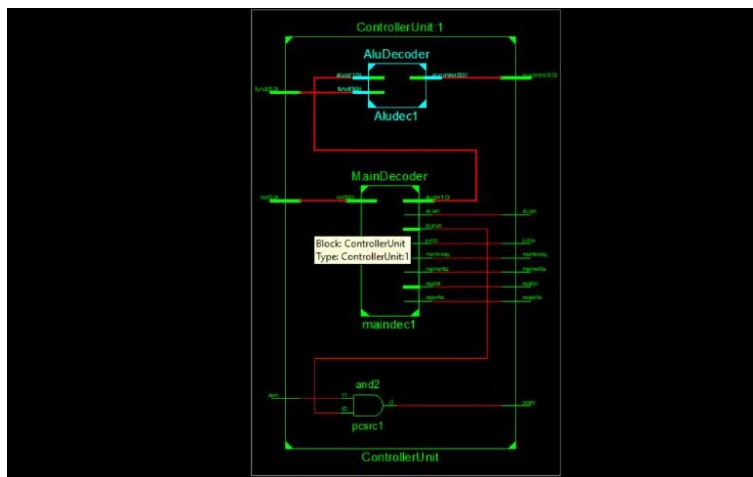


Figure 38:mips RTL schematic

Main module:

```

1 |
2 | library IEEE;
3 | use IEEE.STD_LOGIC_1164.ALL;
4 | use work.mainmodulepack.all;
5 |
6 | entity MainModule is
7 | port( clk , reset : in std_logic;
8 |       writedata , dataadr : out std_logic_vector(31 downto 0);
9 |       memwrite : out std_logic);
10 | end MainModule;
11 |
12 | architecture Behavioral of MainModule is
13 |
14 | signal memwritet : std_logic;
15 | signal pc , instr , readdata , dataadr , writedat : std_logic_vector(31 downto 0);
16 | signal aluout : std_logic_vector(31 downto 0 );
17 |
18 | begin
19 |
20 |
21 | memwrite <= memwritet ;
22 |
23 | dataadr <= aluout;
24 |
25 | writedata <= writedat ;
26 |
27 | mips1 : MIPS port map(clk , reset , pc , instr , memwritet , aluout , writedat , readdata );
28 |
29 | instrmem : imem port map(pc(7 downto 2) , instr);
30 |
31 | datamem : dmem port map(clk , memwritet , aluout , writedat , readdata );
32 |
33 |
34 | end Behavioral;
35 |

```

Figure 39:main module code

main module RTL schematic:

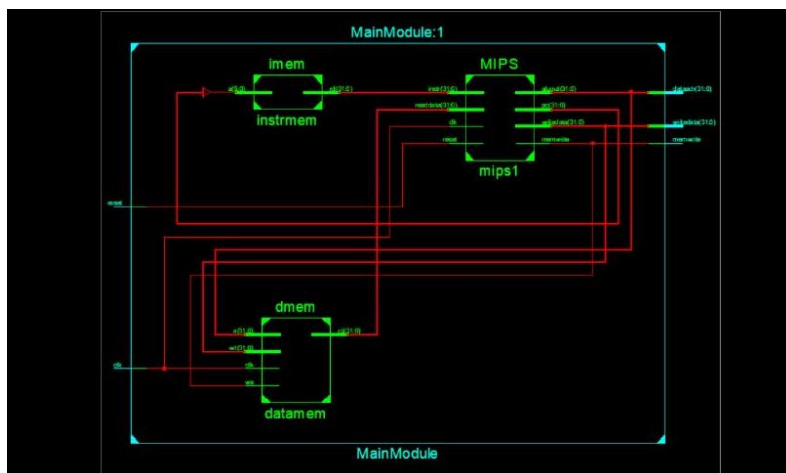


Figure 40:main module RTL schematic

Main module_tb(test bench):

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.all;
3  use IEEE.STD_LOGIC_SIGNED.all;
4  use IEEE.STD_LOGIC_ARITH.all;
5  use ieee.numeric_std.all;
6
7  ENTITY Mainmdoule_tb IS
8  END Mainmdoule_tb;
9
10 ARCHITECTURE behavior OF Mainmdoule_tb IS
11     -- Component Declaration for the Unit Under Test (UUT)
12     COMPONENT MainModule
13     port (clk, reset: in STD_LOGIC;
14           writedata, dataadr: out STD_LOGIC_VECTOR(31 downto 0);
15           memwrite: out STD_LOGIC);
16     end component;
17
18
19     signal writedata, dataadr: STD_LOGIC_VECTOR(31 downto 0);
20     signal clk, reset, memwrite: STD_LOGIC;
21     -- Clock period definitions
22     constant clk_period : time := 10 ns;
23
24 BEGIN
25     dut: MainModule port map(clk, reset, writedata, dataadr, memwrite);
26     -- Generate clock with 10 ns period
27     process begin
28         clk <= '1';
29         wait for 5 ns;
30         clk <= '0';
31         wait for 5 ns;
32     end process;
33     -- Generate reset for first two clock cycles
34     process begin
35         reset <= '1';
36         wait for 22 ns;
37         reset <= '0';
38         wait;
```

Figure 41:main module test bench code1

```
38     wait;
39     end process;
40
41     -- check that 7 gets written to address 84 at end of program
42     process(clk) begin
43         if (clk'event and clk = '0' and memwrite = '1') then
44             if (CONV_INTEGER(dataadr) = 84 and CONV_INTEGER(writedata) = 7) then
45                 report "NO ERRORS: Simulation succeeded" severity failure;
46             elsif (CONV_INTEGER(dataadr) = 84) then
47                 report "Simulation failed" severity failure;
48             end if;
49         end if;
50     end process;
51 end process;
52 end;
```

Figure 42:main module test bench code2

Main module test bench results:

 


Figure 43: main module test bench simulation

Although our implementation was correct bas the test bench results didn't come out as expected.

The Expected Results:

INSTRUCTIONS 1-5: 1ST 5 CYCLES

INSTRUCTIONS 6-10: 2ND 5 CYCLES

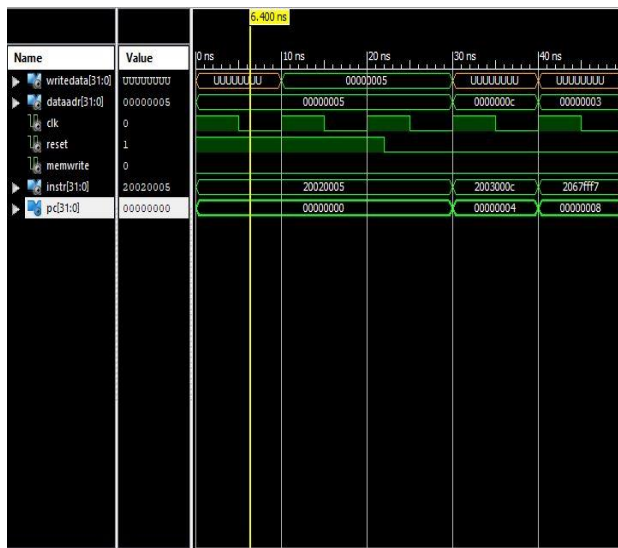


Figure 45: INSTRUCTIONS 1-5: 1ST 5 CYCLES

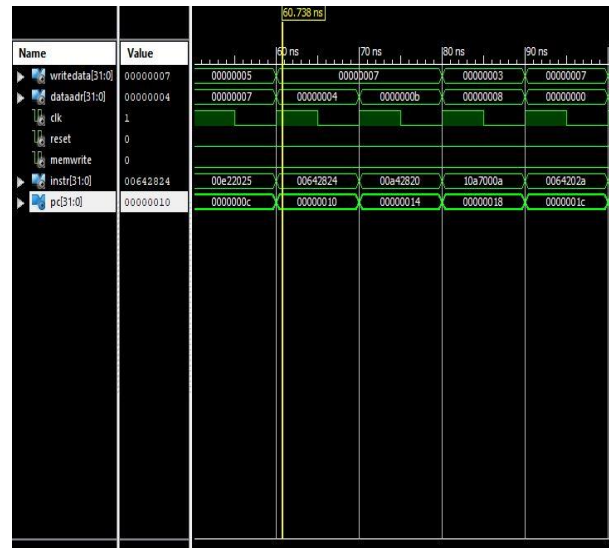


Figure 44: INSTRUCTIONS 6-10: 2ND 5 CYCLES

INSTRUCTIONS 11-15: 3RD 5 CYCLES LAST INSTRUCTION: CYCLE # 16



Figure 46: INSTRUCTIONS 11-15: 3RD 5 CYCLES

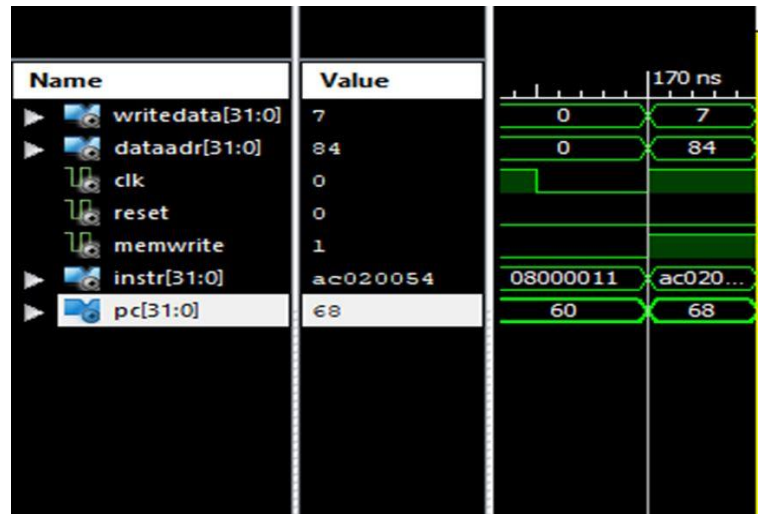


Figure 47: LAST INSTRUCTION: CYCLE # 16

Adder:

```
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.std_logic_unsigned.all;
23
24 -- Uncomment the following library declaration if using
25 -- arithmetic functions with Signed or Unsigned values
26 --use IEEE.NUMERIC_STD.ALL;
27
28 -- Uncomment the following library declaration if instantiating
29 -- any Xilinx primitives in this code.
30 --library UNISIM;
31 --use UNISIM.VComponents.all;
32
33 entity adder is
34 port ( A : in std_logic_vector(31 downto 0);
35       B : in std_logic_vector(31 downto 0);
36       S : out std_logic_vector(31 downto 0));
37 end adder;
38
39 architecture Behavioral of adder is
40 begin
41
42   S <= A + B ;
43
44 end Behavioral;
45
46
```

Figure 48:adder code

Adder RTL schematic:

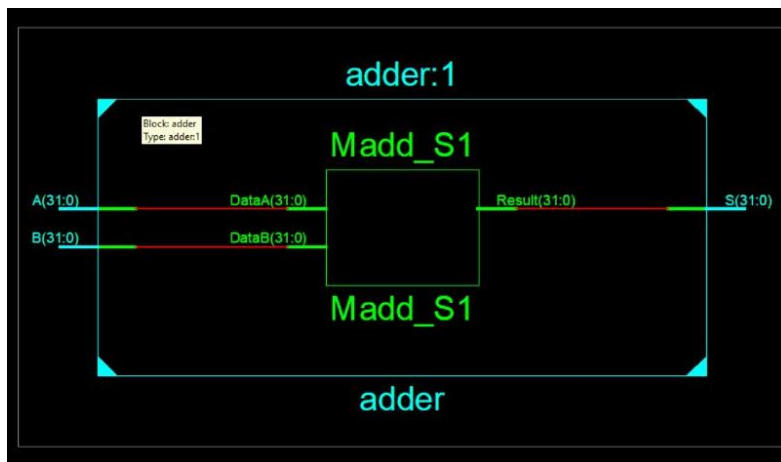


Figure 49:adder RTL schematic

Shifter:

```
14 --  
15 -- Revision:  
16 -- Revision 0.01 - File Created  
17 -- Additional Comments:  
18 --  
19 -----  
20 library IEEE;  
21 use IEEE.STD_LOGIC_1164.ALL;  
22  
23 -- Uncomment the following library declaration if using  
24 -- arithmetic functions with Signed or Unsigned values  
25 --use IEEE.NUMERIC_STD.ALL;  
26  
27 -- Uncomment the following library declaration if instantiating  
28 -- any Xilinx primitives in this code.  
29 --library UNISIM;  
30 --use UNISIM.VComponents.all;  
31  
32 entity Shifter is  
33   Port ( INPUT : in  STD_LOGIC_VECTOR (31 downto 0);  
34         OUTPUT : out STD_LOGIC_VECTOR (31 downto 0));  
35 end Shifter;  
36  
37 architecture Behavioral of Shifter is  
38  
39   begin  
40  
41     OUTPUT <= INPUT( 29 downto 0) & "00" ;  
42  
43   end Behavioral;  
44  
45
```

Figure 50:shifter code

Shifter RTL schematic:

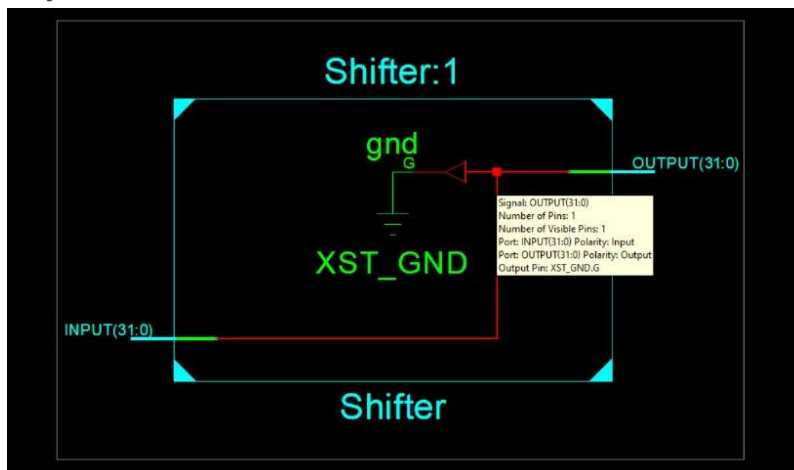


Figure 51:shifter RTL schematic

Sign extend:

```
12 --  
13 -- Dependencies:  
14 --  
15 -- Revision:  
16 -- Revision 0.01 - File Created  
17 -- Additional Comments:  
18 --  
19 -----  
20 library IEEE;  
21 use IEEE.STD_LOGIC_1164.ALL;  
22  
23 -- Uncomment the following library declaration if using  
24 -- arithmetic functions with Signed or Unsigned values  
25 --use IEEE.NUMERIC_STD.ALL;  
26  
27 -- Uncomment the following library declaration if instantiating  
28 -- any Xilinx primitives in this code.  
29 --library UNISIM;  
30 --use UNISIM.VComponents.all;  
31  
32 entity SignedBits is  
33     Port ( INPUT : in  STD_LOGIC_VECTOR (15 downto 0);  
34           OUTPUT : out STD_LOGIC_VECTOR (31 downto 0));  
35 end SignedBits;  
36  
37 architecture Behavioral of SignedBits is  
38  
39     begin  
40  
41     OUTPUT <= X"ffff"& INPUT WHEN INPUT(15)='1' ELSE  
42     X"0000" & INPUT;  
43  
44  
45  
46     end Behavioral;  
47
```

Figure 52:sign extend code

Sign extend RTL schematic:

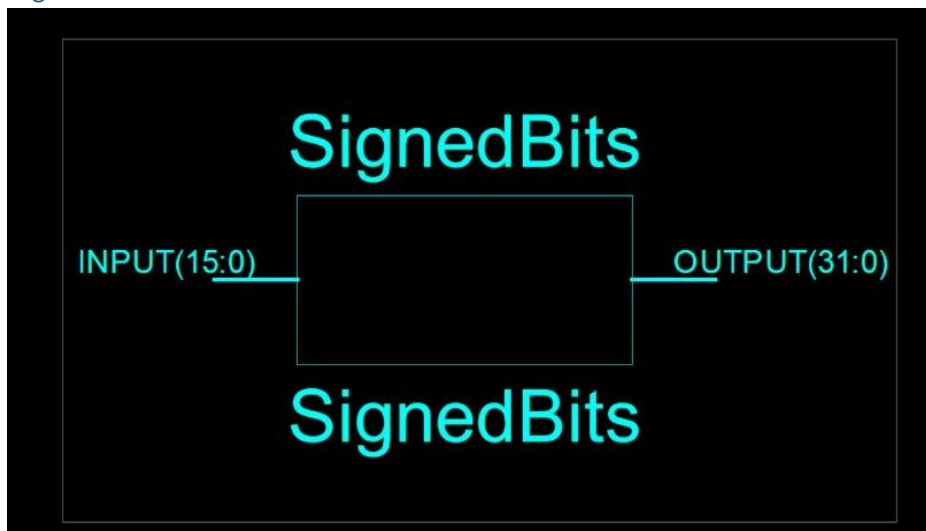


Figure 53:sign extend RTL schematic

MUX 5 bits:

```

15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity MUX2x15bits is
33
34 port( A0 : in std_logic_vector(4 downto 0);
35       A1 : in std_logic_vector(4 downto 0);
36       Z1 : out std_logic_vector(4 downto 0);
37       S : in std_logic);
38 end MUX2x15bits;
39
40 architecture Behavioral of MUX2x15bits is
41
42 begin
43
44   Z1 <= A0 when S='0' else
45         A1 when S='1' ;
46
47 end Behavioral;
48
49

```

Figure 54: MUX code

MUX 5bits RTL schematic:

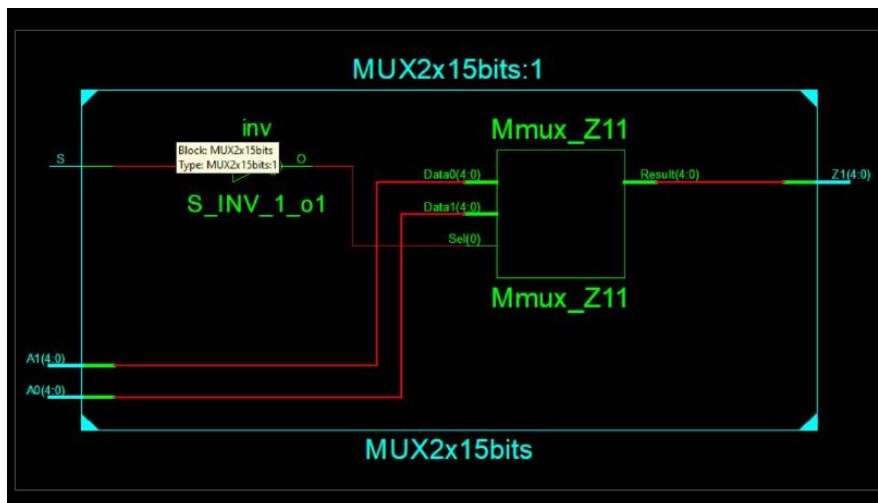


Figure 55: MUX RTL schematic

Instruction memory:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.all;
3  use IEEE.STD_LOGIC_1164.all;
4  use IEEE.STD_LOGIC_SIGNED.all;
5  use IEEE.STD_LOGIC_ARITH.all;
6  use IEEE.numeric_std.all;
7  use IEEE.std_logic_textio.all;
8  library STD;
9  use STD.textio.all;
10 entity imem is -- instruction memory
11 port(a: in STD_LOGIC_VECTOR(5 downto 0);
12      rd: out STD_LOGIC_VECTOR(31 downto 0));
13 end;
14
15 architecture behave of imem is
16 begin
17 process is
18 file mem_file: TEXT;
19 variable L: line;
20 variable ch: character;
21 variable i, index, result: integer;
22 type ramtype is array (63 downto 0) of STD_LOGIC_VECTOR(31 downto 0);
23 variable mem: ramtype;
24 begin
25 -- initialize memory from file
26 for i in 0 to 63 loop -- set all contents low
27 mem(i) := (others => '0');
28 end loop;
29 index := 0;
30 FILE_OPEN(mem_file, "E:\SEM 4\Comp Arch\VHDL\memfile.dat", READ_MODE);
31 while not endfile(mem_file) loop
32 readline(mem_file, L);
33 result := 0;
34 for i in 1 to 8 loop
35 read(L, ch);
36 if '0' <= ch and ch <= '9' then
37 result := character'pos(ch) - character'pos('0');
38 elsif 'a' <= ch and ch <= 'f' then
39 result := character'pos(ch) - character'pos('a') + 10;
40 else report "Format error on line" & integer'
41 image(index) severity error;
42 end if;
43 mem(index) (35-i*4 downto 32-i*4) := std_logic_vector(to_unsigned(result, 4));
44 end loop;
45 index := index + 1;
46 end loop;
47 -- read memory
48 for i in 1 to 1000 loop
49 rd <= mem(CONV_INTEGER(a));
50 wait on a;
51 end loop;
52 end process;
53
54 end;

```

Figure 56:Imem code

Instruction memory RTL schematic:

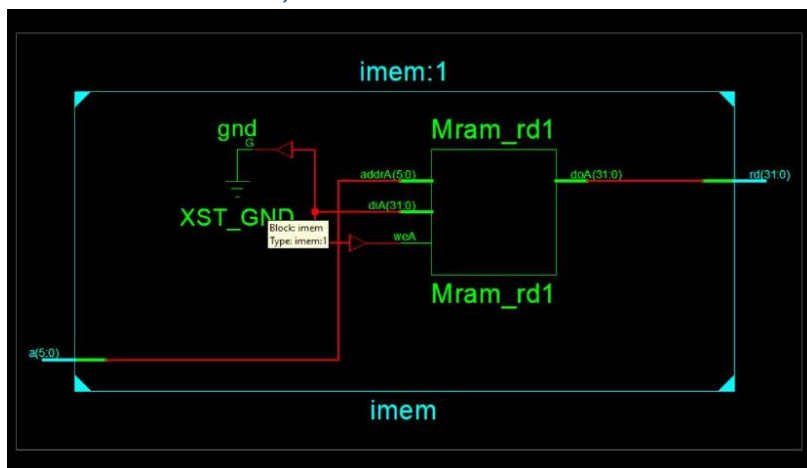


Figure 57:Imem RTL schematic

Data memory:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.all;
3  use IEEE.STD_LOGIC_SIGNED.all;
4  use IEEE.STD_LOGIC_ARITH.all;
5  use IEEE.numeric_std.all;
6
7  entity dmem is -- data memory
8  port(clk, we: in STD_LOGIC;
9  a, wd: in STD_LOGIC_VECTOR (31 downto 0);
10 rd: out STD_LOGIC_VECTOR (31 downto 0));
11 end;
12 architecture behave of dmem is
13 begin
14 process is
15 type ramtype is array (63 downto 0) of STD_LOGIC_VECTOR(31 downto 0);
16 variable mem: ramtype;
17 begin
18 -- read or write memory
19 for i in 1 to 1000 loop
20 if rising_edge(clk) then
21 if (we='1') then
22 mem(CONV_INTEGER('0' & a(7 downto 2))) := wd;
23 end if;
24 end if;
25 rd <= mem (CONV_INTEGER('0' & a (7 downto 2)));
26 wait on clk, a;
27 end loop;
28 end process;
29 end;
30

```

Figure 58:dmem code

Data memory RTL schematic:

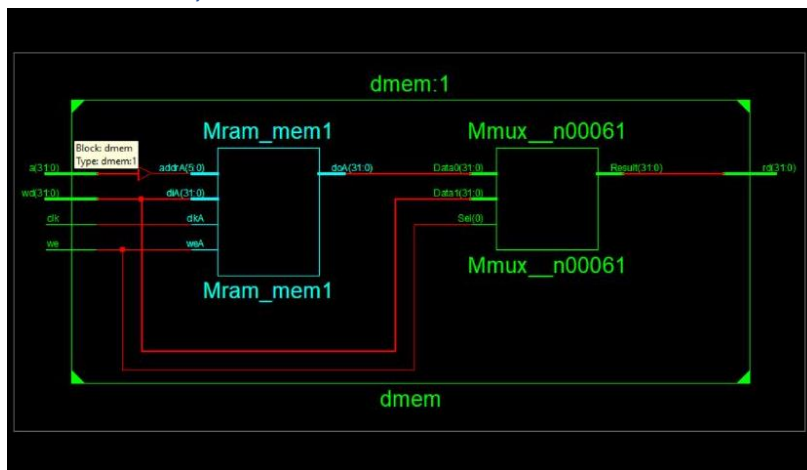


Figure 59:dmem RTL schematic

Code description:

- In phase 2 we implemented the data path consisting of: 5 muxs, shifter, 2 adders and sign extend.
- 1st adder used to increment the pc address by 4.
- 2nd adder used for branch instructions.
- The 1st mux we used was for write register according to the format R, and it will choose the instruction for [15 to 11], according to I format [25-21].
- 2nd mux we used was for the ALU's second input to choose between read data2 and 16-bit sign extend.
- 3rd mux was used to choose between read data from data memory and ALU output to write in the data of the register.
- 4th mux was used to choose between branch and pc next address.
- 5th mux was used to choose between branch mux output (4th mux) and the pc jump in case of the J format.
- Shifter was used for the immediate for I format.
- Sign extend used to make the 16 bits immediate to 32 bits for operations.
- ALU decoder is responsible for control of ALU operations according to its 2 bits.

Instruction	Aluop	funct	alucontrol
lw,sw,addi	00		0010
Beq	01		0110
R-type	10	100000	0010
		100010	0110
		100100	0000
		100101	0001
		101010	0111

Figure 60: ALU decoder table

- ALU decoder and the main decoder are components for the controller unit.

Instruction	op	Regwrite	Regdst	Alusrc	Branch	Mem write	Memtoereg	Jump	Aluop (1)	Aluop (0)
R-type	000000	1	1	0	0	0	0	0	1	0
Lw	100011	1	0	1	0	0	1	0	0	0
Sw	101011	0	0	1	0	1	0	0	0	0
beq	000100	0	0	0	1	0	0	0	0	1
addi	001000	1	0	1	0	0	0	0	0	0
J	000010	0	0	0	0	0	0	1	0	0

Figure 61: Main decoder table

Acknowledgement

Thanks to Dr Karim Emara for your effort through the semester and always providing feedback.

And, Thanks to the TAs Eng Aya and Eng Yasmin for helping us in the major task and their feedback and always being supportive and helpful.